

Printed page: 02

Subject Code: AEC0101 / AMIEC0101

Roll No:

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA

(An Autonomous Institute Affiliated to AKTU, Lucknow)

B.Tech / M.Tech (Integrated)

(SEM: I) SESSIONAL EXAMINATION –III (2020-2021)

Subject Name: Basic Electrical & Electronics Engineering


Time: 1.15Hours

Max. Marks:30

General Instructions:

- All questions are compulsory. Answers should be brief and to the point.
- This Question paper consists of two pages & five questions.
- It comprises of three Sections, A, B, and C. You are to attempt all the sections.
- **Section A** - Question No- 1 is objective type questions carrying 1 mark each, Question No- 2 is very short answer type carrying 2 mark each. You are expected to answer them as directed.
- **Section B** - Question No-3 is Short answer type questions carrying 5 marks each. You need to attempt any two out of three questions given.
- **Section C** - Question No. 4 & 5 are Long answer type (within unit choice) questions carrying 6marks each. You need to attempt any one part a or b.
- Students are instructed to cross the blank sheets before handing over the answer sheet to the invigilator.
- No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

		<u>SECTION – A</u>	[8]	
1.	Answer <u>all</u> questions-		(4×1=4)	
	a.	ELCBs are specially used to disconnect the supply under: i. short circuit condition ii. earth fault condition iii. open circuit condition iv. over load condition	(1)	CO3
	b.	The ripple factor of a full-wave rectifier circuit compared to that of a half wave rectifier circuit without filter is: i. half of that for a half wave rectifier ii. less than half that for a half-wave rectifier circuit iii. equal to that of a half wave rectifier. iv. none of the above.	(1)	CO4
	c.	Which type of sensor is used to measure the distance between the vehicle and other objects in its environment: i. Ultrasonic sensor ii. Tactile sensor iii. Motion sensor iv. None of these	(1)	CO5

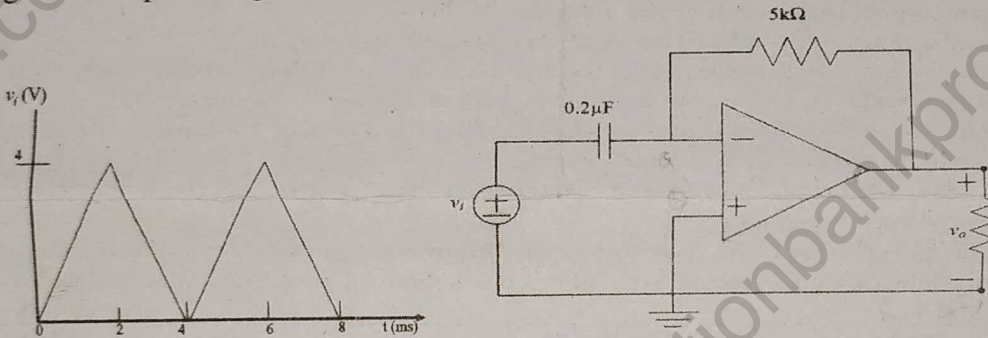	d.	Output Impedance of an ideal op-amp is: i. Infinite ii. Very high iii. Low iv. Zero	(1)	CO5
2.	Answer all questions-		(2×2=4)	
	a.	If a home has 10 tube lights of 30W that run for 4 hours daily, 5 fans of 70W running for 10 hours daily. Calculate total amount to be paid in a month, if the cost per unit is Rs. 7.	(2)	CO3
	b.	What are the advantages of OLED display?	(2)	CO4
SECTION – B				
3.	Answer any two of the following-		[2×5=10]	
	a.	Explain the formation of depletion layer in P-N junction diode and also define barrier potential.	(5)	CO4
	b.	Obtain the expression for output voltage $v_o(t)$ for the circuit shown, given the input voltage waveform below.	(5)	CO5
				
	c.	Give the introduction to Internet of Things (IoT). What impacts will the Internet of Things (IoT) have on the Transportation Sector?	(5)	CO5
SECTION – C				
			[2×6=12]	
4.	Answer any one of the following-			
	a.	Explain the working of center-taped full wave rectifier with diagram. Define Ripple factor and calculate the ripple factor for full wave rectifier.	(6)	CO4
	b.	Define Input bias current and input offset current. If the base currents for the emitter coupled transistors of a differential amplifier are $18\mu A$ and $22\mu A$, determine (i) input bias current (ii) input offset current.	(6)	CO5
5.	Answer any one of the following-			
	a.	What of the need of electrical earthing? Explain different type of earthing used in electrical system.	(6)	CO4
	b.	Draw and explain the positive and negative biased clipper circuits with waveforms. Also explain the combinational clipper circuit.	(6)	CO5