

NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA
(An Autonomous Institute)

Affiliated to Dr. A.P. J. Abdul Kalam Technical University, Uttar Pradesh, Lucknow

Course- B.Tech

Branch- CSE

Semester- 3rd

Third Sessional Examination

Year- (2021 - 2022)

Subject Name: DIGITAL LOGIC & CIRCUIT DESIGN

Time: 1.15Hours


[SET- B]

Max. Marks:30

General Instructions:

- This Question paper consists of 2 pages & 5 questions. It comprises of three Sections, A, B, and C
- **Section A** - Question No- 1 is objective type questions carrying 1 mark each, Question No- 2 is very short answer type carrying 2 mark each. You are expected to answer them as directed.
- **Section B** - Question No-3 is Short answer type questions carrying 5 marks each. Attempt any two out of three questions given.
- **Section C** - Question No. 4 & 5 are Long answer type (within unit choice) questions carrying 6 marks each. Attempt any one part a or b.

SECTION - A			[08Marks]	
1.	All questions are compulsory		(4×1=4)	
a.	How many flip-flops are required to construct a decade counter? (a) 4 (b) 8 (c) 5 (d) 10		(1)	CO3
b.	If present state of JK flip flop is 0 and next state is 1 then input of JK flip flop will be _____ (a) 0 1 (b) 0 0 (c) 1 X (d) 1 0		(1)	CO3
c.	In a 3-bit asynchronous up counter, the initial content is _____ (a) 000 (b) 001 (c) 100 (d) 111		(1)	CO3
d.	The number of clock pulse required to store 4 bit data in a PIPO shift register is _____ (a) 4 (b) 1 (c) 3 (d) none of these		(1)	CO3
2.	All questions are compulsory		(2×2=4)	
a.	What is the difference between Register and counters?		(2)	CO3
b.	Distinguish between Latch and Flip Flop with example		(2)	CO3

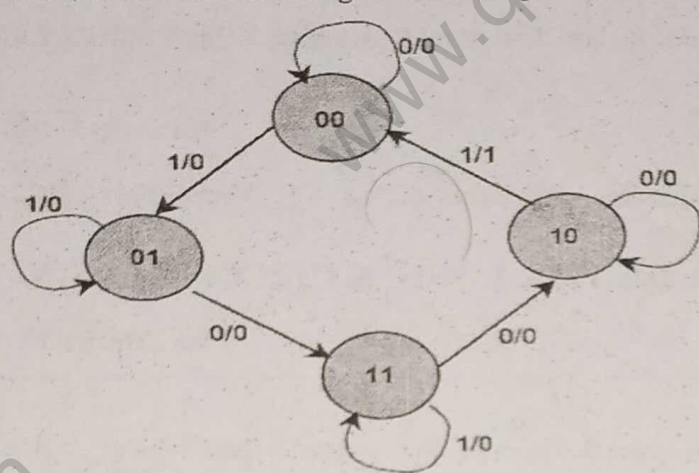SECTION – B			[10Marks]	
3.	Answer any <u>two</u> of the following-		(2×5=10)	
a.	What do you mean by Race around Condition ? How it will be avoided?		(5)	CO3
b.	Draw the basic logic diagram of JK flip flop using NAND gate and find the truth table, characteristic table and excitation table of JK flip flop.		(5)	CO3
c.	Write the state table for the given state diagram		(5)	CO4
				
SECTION – C			[12Marks]	
4	Answer any <u>one</u> of the following-		(1×6=6)	
a.	Design a MOD-6 Asynchronous counter with suitable diagrams		(6)	CO3
b.	For the clocked T- flip flop write the sate table, draw the state diagram and write the state equation		(6)	CO4
5.	Answer any <u>one</u> of the following-		(1×6=6)	
a.	Write the steps for Flip flop conversion and convert JK flip flop to T flip flop.		(6)	CO3
b.	Write the short notes on (i) Ring Counter (ii) Johnson Counter		(6)	CO3