

**NOIDA INSTITUTE OF ENGINEERING AND TECHNOLOGY, GREATER NOIDA**  
**(An Autonomous Institute Affiliated to AKTU, Lucknow)**  
**BACHELOR OF TECHNOLOGY (B.Tech).**

**(SEM: FIRST SEMESTER, THEORY EXAMINATION (2020-2021))**

**SUBJECT NAME: BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

Time: 3 Hours

Max. Marks:100

**General Instructions:**

- All questions are compulsory. Answers should be brief and to the point.
- This Question paper consists of 03 pages & 8 questions.
- It comprises of three Sections, A, B, and C. You are to attempt all the sections.
- **Section A** - Question No- 1 is objective type questions carrying 1 mark each, Question No- 2 is very short answer type carrying 2 mark each. You are expected to answer them as directed.
- **Section B** - Question No-3 is Long answer type-I questions with external choice carrying 6 marks each. You need to attempt any five out of seven questions given.
- **Section C** - Question No.4 to 8 are Long answer type -II (within unit choice) questions carrying 10 marks each. You need to attempt any one part a or b.
- Students are instructed to cross the blank sheets before handing over the answer sheet to the invigilator.
- No sheet should be left blank. Any written material after a blank sheet will not be evaluated/checked.

**SECTION – A****1. Answer all the parts-**


- a. Consider the circuit shown below. Find the equivalent Thevenin's voltage (volts) between nodes A and B

[10×1=10]

CO

(1)

CO1

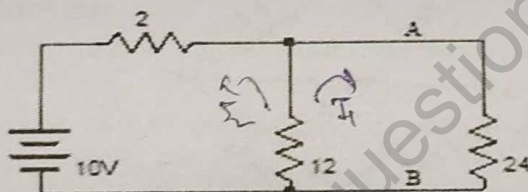

- (A) 8 (B) 8.5 (C) 9 (D) 9.5
- b. In a delta network each element has value R. The value of each element in equivalent star network will be: (1) CO1  
 (A) 3R (B) R/3 (C) R/6 (D) R/12
- c. In a series R, L circuit, voltage across resistor and inductor are 3 V and 4 V respectively, then what is the applied voltage? (1) CO2  
 (A) 7V (B) 1V (C) 5V (D) 25V
- d. In RLC series circuit, if the voltage across capacitor is greater than voltage across inductor, then power factor of the network is: (1) CO2  
 (A) Lagging (B) Leading (C) Unity (D) Zero
- e. Normally the efficiency of a transformer lies in the range of..... (1) CO3
- f. MCB & ELCB stands for.....&.....respectively. (1) CO3
- g. A Zener diode is used as..... (1) CO4  
 (A) an amplifier (B) a rectifier (C) a voltage regulator (D) a multivibrator
- h. If PIV rating of a diode is exceeded, the diode..... (1) CO4  
 (A) stops conduction (B) is destroyed  
 (C) conducts heavily in forward direction (D) None of these

i. An ideal Op-Amp has.....

- (A) Infinite input resistance (B) Infinite voltage gain  
(C) Zero output resistance (D) All of these

(1) CO5

j. Internet domain name and hostname are translated into IP address by.....


- (A) Domain name system (B) Domain name database  
(C) Router (D) Domain information System

[5×2=10] CO

2. Answer all the parts-

(2) CO1

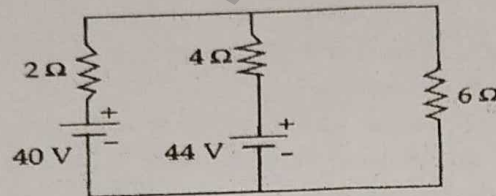a. Calculate the current in  $6\ \Omega$  branch for the circuit shown in Figure given below-



b. An RLC circuit consisting of resistance  $40\ \Omega$ , capacitance  $120\ \mu\text{F}$  and inductance  $5\text{H}$  are connected in series with a supply of  $250\text{V}$ ,  $50\text{Hz}$  source. Calculate quality factor

(2) CO2

c. Explain the principle of operation of a 1-phase Transformer on no-load.

(2) CO3

d. Explain the breakdown mechanism in a diode.

(2) CO4

e. Draw the diagrams of Inverting and Non-inverting Op-Amps.

(2) CO5

### SECTION - B


3. Answer any five of the following-

[5×6=30]

a. Find the equivalent resistance between x-y using star-delta transformation in the Fig.2

(6) CO1

✓ shown.  
Fig.2

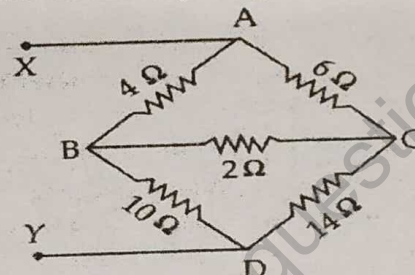

b. State Maximum Power Transfer Theorem applied for DC circuits. Derive its condition also.

(6) CO1

c. The voltage applied to a circuit is  $v = 100 \sin(\theta + 30^\circ)$  and the current flowing in the circuit is  $i = 15 \sin(\theta + 60^\circ)$ . Determine the impedance, resistance, reactance, power and the power factor of the circuit.

(6) CO2

d. What are the necessities and advantages of using 3-phase system? Derive  $V_L = \sqrt{3}V_{ph}$  for star connection.

(6) CO2

e. A  $50\text{KVA}$  transformer is operating at  $0.9$  power factor lagging and  $75\%$  of the full load. Find the efficiency of the transformer if the core and copper losses at full load are  $900\text{W}$  and  $1200\text{W}$  respectively.

(6) CO3

f. Describe a half wave rectifier using a junction diode. Derive the expressions for ripple factor and efficiency for half wave rectifier circuit.

(6) CO4


g. Draw the circuit diagram of an Integrator using Op-Amp and find the expression of output voltage.

(6) CO5




**SECTION - C****Answer any one of the following-**[5×10=50] CO  
(10) CO1

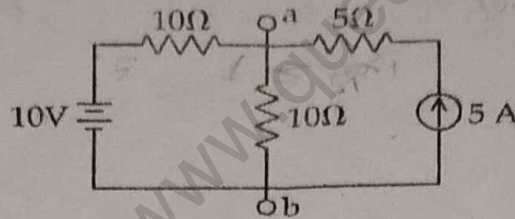- a. Find the Thevenin equivalent model across a-b in Fig.3.



- b. Find the node voltages at node X and Y in the circuit of Fig.4. using Nodal Analysis.

(10) CO1

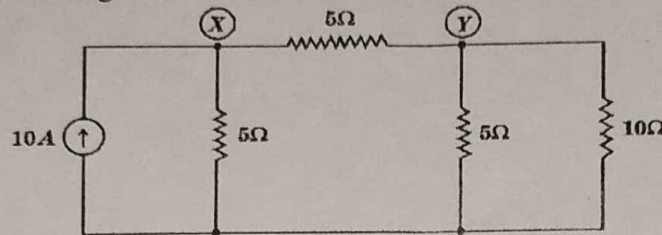**5. Answer any one of the following-**

- a. A series RLC circuit consisting of resistance
- $20\ \Omega$
- , capacitance
- $150\ \mu\text{F}$
- and inductance
- $2\text{H}$
- are connected with
- $250\text{V}$
- ,
- $50\text{Hz}$
- source. Calculate:

(10) CO2

- Power factor
- The frequency of supply to be adjusted to make the power factor unity.
- Net reactance and impedance.

- b. Derive the expression for power in a three-phase star connection. A balanced star connected load of
- $(8+j6)\ \Omega$
- per phase is connected to a balanced 3-phase,
- $400\text{V}$
- supply. Find the line current, power factor and power.

(10) CO2

**6. Answer any one of the following-**

- a. Develop the equivalent circuit of a single-phase transformer on no-load and on-load conditions.

(10) CO3

- b. Draw a one-line diagram of a Power System from generating station to end user. Mention the different voltage levels.

(10) CO3

**7. Answer any one of the following-**

- a. State and explain the characteristics of a Zener diode. How it can be used as a voltage regulator?

(10) CO4

- b. Clearly explain the difference in principle of operation between LED and LCD. Why are LCDs preferred for displays in the pocket calculators?

(10) CO4

**8. Answer any one of the following-**

- a. In a Non-inverting Op-Amp, the value of gain is 1.5. If the input resistance is
- $4\text{k}\Omega$
- , what should be the feedback resistance
- $R_f$
- to have desired gain?

(10) CO5

- b. Find the gain of the amplifier shown in Fig.5. Open loop gain is
- $10^5$
- .

(10) CO5

